

# Digital Logic

## Lecture 18

### Section C.2 (on CD)

Robb T. Koether

Hampden-Sydney College

Wed, Oct 9, 2019

- 1 Digital Logic
- 2 Boolean Algebra
- 3 Truth Tables
- 4 Combinational Circuits
- 5 Assignment

# Outline

- 1 Digital Logic
- 2 Boolean Algebra
- 3 Truth Tables
- 4 Combinational Circuits
- 5 Assignment

- The digital system hierarchy
  - Transistors.
  - Gates and flip-flops.
  - Functional units (registers, memories, arithmetic units, etc.).
  - Systems (e.g., computers).

- Logic systems are **combinational** or **sequential**.
- Combinational systems have no internal memory.
  - The same inputs always produce the same outputs.
- Sequential systems have internal memory.
  - The same inputs may produce different outputs, depending on the values stored.

- A **gate** is a simple electronic system that implements a logical operation.
- The direction of information flow is from the input terminals to the output terminal.
- The number of input and output terminals is finite and they carry binary-valued signals.
- The transformation of input signals to output signals can be modeled by a boolean expression.

- Basic combinatorial circuits
  - AND gate
  - OR gate
  - Inverter (NOT gate)
  - XOR gate
  - Multiplexor
  - Decoder

- Combinatorial circuits can be represented in different ways.
  - Truth tables
  - Boolean expressions
  - Logic diagrams
- We can transform any one of these in any other.




# Buffer

## Buffer

$x$

$x$	$x$
0	0
1	1

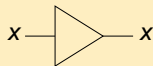

Boolean expression

Truth table


Logic diagram

# NOT Gates

## NOT Gates

$\bar{x}$

$x$	$\bar{x}$
0	1
1	0

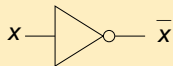

Boolean expression

Truth table


Logic diagram

# AND Gates

## AND Gates

$x \cdot y$

$x$	$y$	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

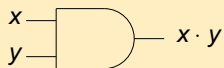

Boolean expression

Truth table

Logic diagram

# NAND Gates

## NAND Gates

$$\overline{x \cdot y}$$

$x$	$y$	$\overline{x \cdot y}$
0	0	1
0	1	1
1	0	1
1	1	0



Boolean expression

Truth table


Logic diagram

# OR Gates

## OR Gates

$x + y$

$x$	$y$	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

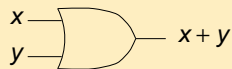

Boolean expression

Truth table


Logic diagram

# NOR Gates

## NOR Gates

$$\overline{x + y}$$

x	y	$\overline{x + y}$
0	0	1
0	1	0
1	0	0
1	1	0

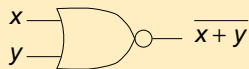

Boolean expression

Truth table


Logic diagram

# XOR Gates

## XOR Gates

$$x \oplus y$$

$x$	$y$	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

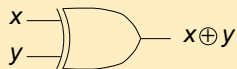

Boolean expression

Truth table

Logic diagram

# NXOR Gates

## NXOR Gates

$$\overline{x \oplus y}$$

$x$	$y$	$\overline{x \oplus y}$
0	0	1
0	1	0
1	0	0
1	1	1



Boolean expression

Truth table

Logic diagram



# Outline

- 1 Digital Logic
- 2 Boolean Algebra**
- 3 Truth Tables
- 4 Combinational Circuits
- 5 Assignment

- In **boolean algebra**
  - There are two **boolean values**: 1 and 0 (or true and false).
  - Variables take on only those values.
  - There are two **binary operators**:  $+$  and  $\cdot$ , representing “and” and “or.”
  - There is one **unary operator**:  $\bar{\phantom{x}}$ , representing “not.”
  - There are 19 **axioms**, defining the behavior of the operators.
- The axioms exhibit **duality**: Each axiom has its dual, by reversing  $+$  and  $\cdot$  and reversing 1 and 0.

# Boolean Algebra Basic Properties

- Commutativity

Boolean Algebra	C++
$a + b = b + a$	<code>a + b == b + a</code>
$a \cdot b = b \cdot a$	<code>a*b == b*a</code>

- Associativity

Boolean Algebra	C++
$(a + b) + c = a + (b + c)$	<code>(a + b) + c == a + (b + c)</code>
$(a \cdot b) \cdot c = a \cdot (b \cdot c)$	<code>(a*b)*c == a*(b*c)</code>

- Distributivity

Boolean Algebra	C++
$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$	<code>a*(b + c) == a*b + a*c</code>
$a + (b \cdot c) = (a + b) \cdot (a + c)$	Oops!

# Boolean Algebra Basic Properties

- Idempotence

Boolean Algebra	C++
$a + a = a$	<code>a    a == a</code>
$a \cdot a = a$	<code>a &amp;&amp; a == a</code>

- Identity

Boolean Algebra	C++
$a + 0 = a$	<code>a    <b>false</b> == a</code>
$a \cdot 1 = a$	<code>a &amp;&amp; <b>true</b> == a</code>

- Annihilation

Boolean Algebra	C++
$a + 1 = 1$	<code>a    <b>true</b> == <b>true</b></code>
$a \cdot 0 = 0$	<code>a &amp;&amp; <b>false</b> == <b>false</b></code>

# Boolean Algebra Basic Properties

- Complementation

Boolean Algebra	C++
$a + \bar{a} = 1$	<code>a    !a == true</code>
$a \cdot \bar{a} = 0$	<code>a &amp;&amp; !a == false</code>

- DeMorgan's Laws

Boolean Algebra	C++
$\overline{a + b} = \bar{a} \cdot \bar{b}$	<code>!(a    b) == !a &amp;&amp; !b</code>
$\overline{a \cdot b} = \bar{a} + \bar{b}$	<code>!(a &amp;&amp; b) == !a    !b</code>

- Absorption

Boolean Algebra	C++
$a \cdot (a + b) = a$	<code>a &amp;&amp; (a    b) == a</code>
$a + (a \cdot b) = a$	<code>a    (a &amp;&amp; b) == a</code>

# Boolean Algebra Basic Properties

- Double negation (self-dual)

Boolean Algebra	C++
$\overline{\overline{a}} = a$	<code>!!a == a</code>

# Outline

- 1 Digital Logic
- 2 Boolean Algebra
- 3 Truth Tables**
- 4 Combinational Circuits
- 5 Assignment

# Truth Tables

## Truth Tables

Input Variables	Output Variables
⋮	⋮

- Create one column for each input variable and one column for each output variable (or expression).
- In the input columns, list every possible combination of values.
- In the output columns, write the computed values.



# Truth Tables

## Example (Two Inputs, Two Outputs)

Input		Intermediate		Output	
$x$	$y$	$x \cdot y$	$x + y$	$x \cdot y + y$	$(x + y) \cdot y$
0	0	0	0	0	0
0	1	0	1	1	1
1	0	0	1	0	0
1	1	1	1	1	1

- Note that this example demonstrates that

$$x \cdot y + y = (x + y) \cdot y$$

# Truth Tables

## Example (Three Inputs, One Output)

Input			Intermediate	Output
$x$	$y$	$z$	$x + y$	$(x + y) \cdot z$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	1	0
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	1	1

# Outline

- 1 Digital Logic
- 2 Boolean Algebra
- 3 Truth Tables
- 4 Combinational Circuits**
- 5 Assignment

# Combinational Circuits

## Example (Combinational Circuit)

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- Using AND, OR, and NOT gates, write a boolean expression for this function.

# Combinational Circuits

- We may begin by writing the expression in **disjunctive normal form**:
  - A **disjunction** of **clauses**.
  - Each clause is a **conjunction** of **literals**, exactly one literal for each input.
  - Each literal is either an input variable or is inverse ( $x$  or  $\bar{x}$ ).
- The disjunctive normal form in this example is

$$\bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC.$$

- Then simplify the expression using the rules of Boolean algebra.

# Combinational Circuits

## Example (Combinational Circuit)

$$\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + ABC + \overline{A}BC$$

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + AB\overline{C} + ABC \\ = \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C)\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1\end{aligned}$$



# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B)\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B) \\ &= \overline{A}BC + A \cdot 1\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B) \\ &= \overline{A}BC + A \cdot 1 \\ &= \overline{A}BC + A\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B) \\ &= \overline{A}BC + A \cdot 1 \\ &= \overline{A}BC + A \\ &= (\overline{A} + A)(BC + A)\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B) \\ &= \overline{A}BC + A \cdot 1 \\ &= \overline{A}BC + A \\ &= (\overline{A} + A)(BC + A) \\ &= 1 \cdot (BC + A)\end{aligned}$$

# Combinational Circuits

## Example (Combinational Circuit)

$$\begin{aligned}\overline{A}BC + A\overline{B}C + A\overline{B}C + AB\overline{C} + ABC \\ &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\ &= \overline{A}BC + A\overline{B} \cdot 1 + AB \cdot 1 \\ &= \overline{A}BC + A\overline{B} + AB \\ &= \overline{A}BC + A(\overline{B} + B) \\ &= \overline{A}BC + A \cdot 1 \\ &= \overline{A}BC + A \\ &= (\overline{A} + A)(BC + A) \\ &= 1 \cdot (BC + A) \\ &= BC + A.\end{aligned}$$

## Example (Combinational Circuit)

$$\overline{ABC} + \overline{A}BC + A\overline{B}C$$

- Or we could find the complementary expression and then invert it.



## Example (Combinational Circuit)

$$\overline{ABC} + \overline{A}BC + A\overline{B}\overline{C} = \overline{A}(\overline{BC} + \overline{BC} + \overline{BC})$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC})\end{aligned}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C})\end{aligned}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C}) \\ &= \overline{A}(\overline{B} + \overline{C}).\end{aligned}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C}) \\ &= \overline{A}(\overline{B} + \overline{C}).\end{aligned}$$

$$\overline{\overline{A}(\overline{B} + \overline{C})}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C}) \\ &= \overline{A}(\overline{B} + \overline{C}).\end{aligned}$$

$$\overline{\overline{A}(\overline{B} + \overline{C})} = \overline{\overline{A}} + \overline{(\overline{B} + \overline{C})}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C}) \\ &= \overline{A}(\overline{B} + \overline{C}).\end{aligned}$$

$$\begin{aligned}\overline{\overline{A}(\overline{B} + \overline{C})} &= \overline{\overline{A}} + \overline{(\overline{B} + \overline{C})} \\ &= A + \overline{\overline{B}} \cdot \overline{\overline{C}}\end{aligned}$$

- Or we could find the complementary expression and then invert it.

## Example (Combinational Circuit)

$$\begin{aligned}\overline{ABC} + \overline{ABC} + \overline{ABC} &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{BC} + \overline{BC} + \overline{BC} + \overline{BC}) \\ &= \overline{A}(\overline{B}(\overline{C} + C) + (B + \overline{B})\overline{C}) \\ &= \overline{A}(\overline{B} + \overline{C}).\end{aligned}$$

$$\begin{aligned}\overline{\overline{A}(\overline{B} + \overline{C})} &= \overline{\overline{A}} + \overline{(\overline{B} + \overline{C})} \\ &= A + \overline{\overline{B}} \cdot \overline{\overline{C}} \\ &= A + BC.\end{aligned}$$

- Or we could find the complementary expression and then invert it.



## Example (Combinational Circuits)

A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Find a boolean expression for this circuit.

## Example (Combinational Circuits)

A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Find a boolean expression for this circuit.

# Outline

- 1 Digital Logic
- 2 Boolean Algebra
- 3 Truth Tables
- 4 Combinational Circuits
- 5 Assignment**

# Assignment

## Assignment

- Read Section C.2 (on CD).