

Addition

Lecture 20 Section C.5

Robb T. Koether

Hampden-Sydney College

Wed, Oct 16, 2019

- 1 Binary Addition
- 2 The Half Adder
- 3 The Full Adder
- 4 The Ripple Adder
- 5 Assignment

Outline

- 1 Binary Addition
- 2 The Half Adder
- 3 The Full Adder
- 4 The Ripple Adder
- 5 Assignment

Binary Addition

8-Bit Addition

```
  0010 1110
+0100 1001
-----
  0111 0111
```

- We apply the grade-school addition algorithm to the binary number system.

Binary Addition

One-Bit Addition

$$0 + 0 = 0,$$

$$0 + 1 = 1,$$

$$1 + 0 = 1,$$

$$1 + 1 = 10.$$

- The rules are very simple.
- Note that in the last case we carry a 1.

One-Bit Addition

One-Bit Addition

a	b	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Adding two bits produces a **sum** bit s and a **carry** bit c .
- Do you recognize the sum and carry as logical functions?

Outline


- 1 Binary Addition
- 2 The Half Adder**
- 3 The Full Adder
- 4 The Ripple Adder
- 5 Assignment

The Half Adder

- A **half adder** is an electronic circuit that receives two bits as input, adds them, and produces the sum and carry bits.
- The sum bit is $s = a \text{ XOR } b$.
- The carry-out bit is $c = a \text{ AND } b$.

The Half Adder


The Half Adder

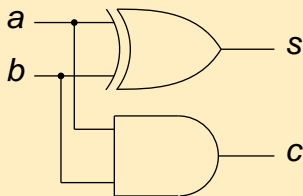

- A **half adder** is an electronic circuit that receives two bits as input, adds them, and produces the sum and carry bits.
- The sum bit is $s = a \text{ XOR } b$.
- The carry-out bit is $c = a \text{ AND } b$.

The Half Adder

The Half Adder

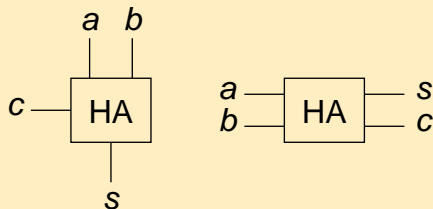

- We will represent a half adder as shown above.

Outline

- 1 Binary Addition
- 2 The Half Adder
- 3 The Full Adder**
- 4 The Ripple Adder
- 5 Assignment

Multi-column Addition

8-Bit Addition

```
00001 000 (carry)
  0010 1110
+0100 1001
-----
0111 0111
```

- Adding more than single bits requires more than a half adder.
- In addition to the two bits in each column, there is the carry bit from the previous column.
- Now each column has a **carry-in** c_{in} and a **carry-out** c_{out} .

Multi-column Addition

8-Bit Addition

```
00001 0000 (carry)
 0010 1110
+0100 1001
-----
0111 0111
```

- Adding more than single bits requires more than a half adder.
- In addition to the two bits in each column, there is the carry bit from the previous column.
- Now each column has a **carry-in** c_{in} and a **carry-out** c_{out} .

Multi-column Addition

One-Bit Addition with Carry-in

a	b	c_{in}	s	c_{out}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Binary Addition

One-Bit Addition

$$\begin{aligned}s &= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc \\ &= (a\bar{b} + \bar{a}b)\bar{c} + (\bar{a}\bar{b} + ab)c \\ &= (a\bar{b} + \bar{a}b)\bar{c} + \overline{(a\bar{b} + \bar{a}b)}c \\ &= (a \oplus b)\bar{c} + \overline{(a \oplus b)}c \\ &= (a \oplus b) \oplus c\end{aligned}$$

- The table allows us to write a Boolean expression for s .
- “ \oplus ” is the symbol for XOR.

Binary Addition

One-Bit Addition

$$\begin{aligned} s &= a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc \\ &= (a\bar{b} + \bar{a}b)\bar{c} + (\bar{a}\bar{b} + ab)c \\ &= (a\bar{b} + \bar{a}b)\bar{c} + \overline{(a\bar{b} + \bar{a}b)}c \\ &= (a \oplus b)\bar{c} + \overline{(a \oplus b)}c \\ &= (a \oplus b) \oplus c \\ &= S_{(a,b)} \oplus c. \end{aligned}$$

- The table allows us to write a Boolean expression for s .
- “ \oplus ” is the symbol for XOR.

Binary Addition


One-Bit Addition

$$\begin{aligned}c_{\text{out}} &= ab\bar{c} + \bar{a}bc + \bar{a}bc + abc \\ &= (abc + ab\bar{c}) + (abc + \bar{a}bc) + (abc + \bar{a}bc) \\ &= ab(c + \bar{c}) + ac(b + \bar{b}) + bc(a + \bar{a}) \\ &= ab + ac + bc.\end{aligned}$$

- We can write a Boolean expression for c_{out} .

The Full Adder

The Full Adder

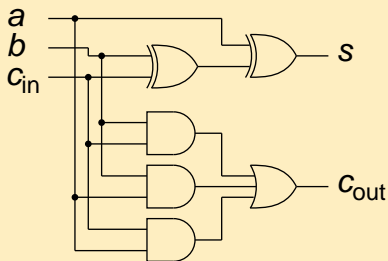

- The above circuit implements the Boolean expressions.

Binary Addition

One-Bit Addition

$$\begin{aligned}c_{\text{out}} &= ab\bar{c} + a\bar{b}c + \bar{a}bc + abc \\ &= (abc + ab\bar{c}) + (a\bar{b}c + \bar{a}bc) \\ &= ab(c + \bar{c}) + (a\bar{b} + \bar{a}b)c \\ &= ab + (a \oplus b)c\end{aligned}$$

- Or we can simplify it this way.

Binary Addition


One-Bit Addition

$$\begin{aligned}c_{\text{out}} &= ab\bar{c} + a\bar{b}c + \bar{a}bc + abc \\ &= (abc + ab\bar{c}) + (a\bar{b}c + \bar{a}bc) \\ &= ab(c + \bar{c}) + (a\bar{b} + \bar{a}b)c \\ &= ab + (a \oplus b)c \\ &= C_{(a,b)} + S_{(a,b)}C.\end{aligned}$$

- Or we can simplify it this way.

The Full Adder


The Full Adder

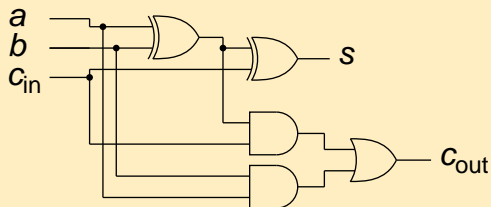

- The second form uses fewer gates.

The Full Adder


The Full Adder

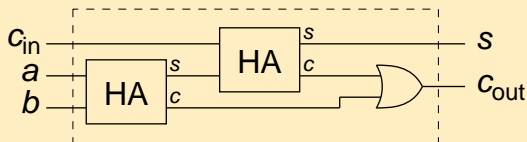

- The simplified circuit can be implemented with two half adders.
- We call this a **full adder**.

The Full Adder

The Full Adder

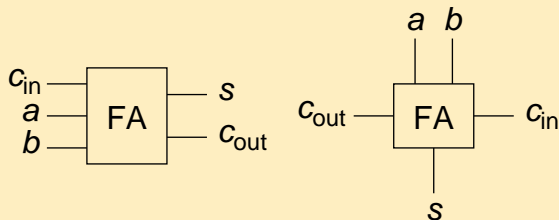


- We can represent it in a variety of ways.

Outline

- 1 Binary Addition
- 2 The Half Adder
- 3 The Full Adder
- 4 The Ripple Adder**
- 5 Assignment

The Ripple Adder


The Ripple Adder

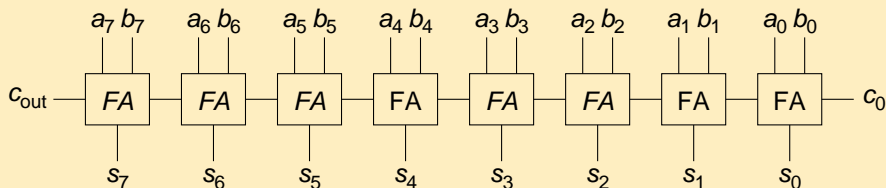

- We can implement multi-column binary addition by using a full adder in each column.
- As one full adder computes its carry-out bit, that bit is used as the carry-in bit of the next full adder.
- This is called a **ripple adder**.

The Ripple Adder

The Ripple Adder

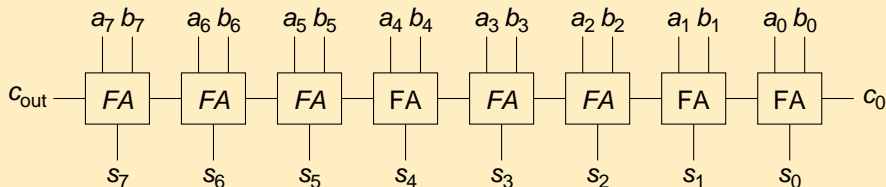

- How many levels of logic (gates) are required by an 8-bit ripple adder?
- How many levels of logic (gates) are required by a 32-bit ripple adder?
- Can we do better?

Outline

- 1 Binary Addition
- 2 The Half Adder
- 3 The Full Adder
- 4 The Ripple Adder
- 5 Assignment**

Assignment

Assignment

- Read Section C.5.