

The Look-Ahead Adder

Lecture 22
Section C.6

Robb T. Koether

Hampden-Sydney College

Wed, Oct 23, 2019

- 1 Look-Ahead Adders
- 2 Propagate and Generate
- 3 A 16-bit Adder
- 4 Subtraction
- 5 Assignment

Outline

- 1 Look-Ahead Adders
- 2 Propagate and Generate
- 3 A 16-bit Adder
- 4 Subtraction
- 5 Assignment

The Carry Bits

- In the case of the ripple adder, we saw some of the operations could be done simultaneously, such as adding a_i and b_i .
- Other operations had to wait for the carry-in bit from the previous column.
- The **look-ahead adder** pushes this idea much further.
- It puts a premium on computing the carry-in bits for all columns as quickly as possible.

Outline

- 1 Look-Ahead Adders
- 2 Propagate and Generate**
- 3 A 16-bit Adder
- 4 Subtraction
- 5 Assignment

The Carry Bits

- In the case of the ripple adder, we saw that the carry-out bit may be computed as

$$ab + ac + bc,$$

where a and b are the two bits to be added and c is the carry-in bit.

- This formula will give the carry-out bit for each column of a multi-bit adder.

The Carry Bits

The Carry Bits

$$c_0 = 0,$$

$$c_1 = b_0c_0 + a_0c_0 + a_0b_0 = (a_0 + b_0)c_0 + a_0b_0,$$

$$c_2 = b_1c_1 + a_1c_1 + a_1b_1 = (a_1 + b_1)c_1 + a_1b_1,$$

$$c_3 = b_2c_2 + a_2c_2 + a_2b_2 = (a_2 + b_2)c_2 + a_2b_2,$$

$$c_4 = b_3c_3 + a_3c_3 + a_3b_3 = (a_3 + b_3)c_3 + a_3b_3,$$

⋮

- c_i represents the carry-in bit and c_{i+1} is the carry-out bit for the i -th column.

The Carry Bits

The Carry Bits

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0,$$

$$\begin{aligned} c_2 &= b_1(b_0 c_0 + a_0 c_0 + a_0 b_0) + a_1(b_0 c_0 + a_0 c_0 + a_0 b_0) + a_1 b_1, \\ &= b_1 b_0 c_0 + b_1 a_0 c_0 + b_1 a_0 b_0 + a_1 b_0 c_0 + a_1 a_0 c_0 + a_1 a_0 b_0 + a_1 b_1, \\ &\text{etc.} \end{aligned}$$

- We may substitute the formula for c_1 into the expression for c_2 , and so on.
- Thus, we may express each c_i in terms of the a_i 's, b_i 's, and c_0 .
- This will quickly get out of hand.

The Generate and Propagate Bits

The Generate and Propagate Bits

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i,$$

$$g_i = a_i b_i,$$

$$p_i = a_i + b_i.$$

- Instead, we will calculate the **generate** and **propagate** bits.
- In column i , a carry of 1 is *generated* if $a_i b_i = 1$.
- In column i , a carry of 1 is *propagated* from the previous column if $a_i + b_i = 1$.

The Generate and Propagate Bits

The Carry Bits

$$c_{i+1} = g_i + p_i c_i.$$

- The carry bit c_{i+1} is 1 if, in the i -th column, either
 - Generates a carry ($g_i = 1$), or
 - Propagates a carry ($p_i = 1$) from the previous column ($c_i = 1$), or
 - Both.

The Generate and Propagate Bits

The Carry Bits

$$c_0 = c_0,$$

$$c_1 = g_0 + p_0 c_0,$$

$$c_2 = g_1 + p_1 c_1$$

$$= g_1 + p_1 (g_0 + p_0 c_0)$$

$$= g_1 + p_1 g_0 + p_1 p_0 c_0,$$

$$c_3 = g_2 + p_2 c_2$$

$$= g_2 + p_2 (g_1 + p_1 g_0 + p_1 p_0 c_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0,$$

- We now have more compact expressions for c_i in terms of c_0 .

The Generate and Propagate Bits

The Carry Bits

$$\begin{aligned}c_4 &= g_3 + p_3 c_3, \\ &= g_3 + p_3(g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0) \\ &= g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0, \\ &\text{etc.}\end{aligned}$$

- We now have more compact expressions for c_i in terms of c_0 .

The Generate and Propagate Bits

- Using the logic of the generate and propagate bits, we first compute $g_i = a_i b_i$ and $p_i = a_i + b_i$ for all columns simultaneously.
- We can see that c_1 through c_4 can be calculated using only 5 more levels of logic.

A Four-bit Adder

1				
p_0				
g_0				
p_1				
g_1				
p_2				
g_2				
p_3				
g_3				

- Using the logic of the generate and propagate bits, we first compute $a_i b_i$ and $a_i + b_i$ for all positions simultaneously.
- How many levels of logic are required to compute $s_0, s_1, s_2, s_3,$ and c_4 ?

A Four-bit Adder

1	2			
p_0	$p_0 c_0$			
g_0	$p_1 g_0$			
p_1	$p_2 g_1$			
g_1	$p_3 g_2$			
p_2	$p_2 p_1$			
g_2	$p_3 p_2$			
p_3	\vdots			
g_3				

- Using the logic of the generate and propagate bits, we first compute $a_i b_i$ and $a_i + b_i$ for all positions simultaneously.
- How many levels of logic are required to compute $s_0, s_1, s_2, s_3,$ and c_4 ?

A Four-bit Adder

1	2	3		
p_0	$p_0 c_0$	$p_1(p_0 c_0)$		
g_0	$p_1 g_0$	$p_2(p_1 g_0)$		
p_1	$p_2 g_1$	$p_3(p_2 g_1)$		
g_1	$p_3 g_2$	$g_1 + (p_1 g_0)$		
p_2	$p_2 p_1$	$g_2 + (p_2 g_1)$		
g_2	$p_3 p_2$	$g_3 + (p_3 g_2)$		
p_3	\vdots	$(p_2 p_1)(p_0 c_0)$		
g_3		\vdots		

- Using the logic of the generate and propagate bits, we first compute $a_i b_i$ and $a_i + b_i$ for all positions simultaneously.
- How many levels of logic are required to compute $s_0, s_1, s_2, s_3,$ and c_4 ?

A Four-bit Adder

1	2	3	4	
p_0	$p_0 c_0$	$p_1(p_0 c_0)$	$p_3(p_2 p_1 p_0 c_0)$	
g_0	$p_1 g_0$	$p_2(p_1 g_0)$	$(g_1 + p_1 g_0) + (p_1 p_0 c_0)$	
p_1	$p_2 g_1$	$p_3(p_2 g_1)$	$(g_2 + p_2 g_1) + (p_2 p_1 g_0)$	
g_1	$p_3 g_2$	$g_1 + (p_1 g_0)$	$(g_3 + p_3 g_2) + (p_3 p_2 g_1)$	
p_2	$p_2 p_1$	$g_2 + (p_2 g_1)$	\vdots	
g_2	$p_3 p_2$	$g_3 + (p_3 g_2)$		
p_3	\vdots	$(p_2 p_1)(p_0 c_0)$		
g_3		\vdots		

- Using the logic of the generate and propagate bits, we first compute $a_i b_i$ and $a_i + b_i$ for all positions simultaneously.
- How many levels of logic are required to compute $s_0, s_1, s_2, s_3,$ and c_4 ?

A Four-bit Adder

1	2	3	4	etc.
p_0	$p_0 c_0$	$p_1(p_0 c_0)$	$p_3(p_2 p_1 p_0 c_0)$...
g_0	$p_1 g_0$	$p_2(p_1 g_0)$	$(g_1 + p_1 g_0) + (p_1 p_0 c_0)$...
p_1	$p_2 g_1$	$p_3(p_2 g_1)$	$(g_2 + p_2 g_1) + (p_2 p_1 g_0)$...
g_1	$p_3 g_2$	$g_1 + (p_1 g_0)$	$(g_3 + p_3 g_2) + (p_3 p_2 g_1)$...
p_2	$p_2 p_1$	$g_2 + (p_2 g_1)$	\vdots	
g_2	$p_3 p_2$	$g_3 + (p_3 g_2)$		
p_3	\vdots	$(p_2 p_1)(p_0 c_0)$		
g_3		\vdots		

- Using the logic of the generate and propagate bits, we first compute $a_i b_i$ and $a_i + b_i$ for all positions simultaneously.
- How many levels of logic are required to compute $s_0, s_1, s_2, s_3,$ and c_4 ?

Outline


- 1 Look-Ahead Adders
- 2 Propagate and Generate
- 3 A 16-bit Adder**
- 4 Subtraction
- 5 Assignment

A 16-bit Adder

- It is not practical to continue in this manner through 16 bits, to say nothing of 32 bits or 64 bits.
- Instead, we view the four-bit adder as a unit.
- A 16-bit adder consists of 4 such units.
- Each unit has its own carry-in and carry-out bits.
- We apply the same logic to these 4 units.

A 16-bit Adder

A Four-bit Adder

 

A 16-bit Adder

Higher-level Generate and Propagate Bits

$$C_0 = c_0,$$

$$P_0 = p_3 p_2 p_1 p_0,$$

$$G_0 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0.$$

- The 4-bit adder may generate the carry bit c_4 or it may propagate it from c_0 .
- We define P_0 and G_0 as shown above.
- Then we compute c_4 as

$$C_1 = G_0 + P_0 C_0.$$

A 16-bit Adder

Higher-level Generate and Propagate Bits

$$C_0 = c_0,$$

$$P_0 = p_3 p_2 p_1 p_0,$$

$$G_0 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0,$$


$$C_1 = c_4$$

$$= g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0,$$

$$= G_0 + P_0 C_0.$$

A 16-bit Adder


A 4-bit Adder

 

- Therefore, the 4-bit adder will output P_0 and G_0 instead of c_4 .

A 16-bit Adder


Four 4-bit Adders

 

- Join together four such units.

A 16-bit Adder

A 16-bit Adder

 

- Add the carry look-ahead unit to compute the carry-in to each 4-bit adder.
- The final carry C_4 is the carry-out of the 16-bit adder.

A 64-bit Adder

- How would we design a 32-bit look-ahead adder?
- How would we design a 64-bit look-ahead adder?

Outline

- 1 Look-Ahead Adders
- 2 Propagate and Generate
- 3 A 16-bit Adder
- 4 Subtraction**
- 5 Assignment

Assignment

Assignment

- Read Section C.6.