

# Sequential Circuits

Lecture 27  
Section C.8

Robb T. Koether

Hampden-Sydney College

Mon, Nov 4, 2019

- 1 Sequential Circuits
- 2 SR Latches
- 3 The Clock
- 4 D Latches
- 5 D Flip Flops
- 6 Assignment

# Outline

1 Sequential Circuits

2 SR Latches

3 The Clock

4 D Latches

5 D Flip Flops

6 Assignment

# Sequential Circuits

- A **sequential circuit** has the ability to store a value.

# Sequential Circuits

- A **sequential circuit** has the ability to store a value.
- Consequently, the output is not fully determined by the input.

# Sequential Circuits

- A **sequential circuit** has the ability to store a value.
- Consequently, the output is not fully determined by the input.
- It is determined by the input together with the stored value(s).

# Sequential Circuits

- A **sequential circuit** has the ability to store a value.
- Consequently, the output is not fully determined by the input.
- It is determined by the input together with the stored value(s).
- This forms the basis of the computer's ability to store data.

# Outline

1 Sequential Circuits

**2 SR Latches**

3 The Clock

4 D Latches

5 D Flip Flops

6 Assignment



# SR Latches

- An **SR latch** is a sequential circuit that has the ability to *store* a bit.

# SR Latches

- An **SR latch** is a sequential circuit that has the ability to *store* a bit.
- Thus, it is a **sequential** circuit.

# SR Latches

- An **SR latch** is a sequential circuit that has the ability to *store* a bit.
- Thus, it is a **sequential** circuit.
- It is also an **unlocked** circuit, meaning that the computer's **clock** (0 or 1) is not one of its inputs.

# SR Latches


- An **SR latch** is a sequential circuit that has the ability to *store* a bit.
- Thus, it is a **sequential** circuit.
- It is also an **unlocked** circuit, meaning that the computer's **clock** (0 or 1) is not one of its inputs.
- It uses two NOR gates whose outputs are fed back in as inputs.

# SR Latches

- An **SR latch** is a sequential circuit that has the ability to *store* a bit.
- Thus, it is a **sequential** circuit.
- It is also an **unlocked** circuit, meaning that the computer's **clock** (0 or 1) is not one of its inputs.
- It uses two NOR gates whose outputs are fed back in as inputs.
- (All sequential circuits use feedback.)

# SR Latches

## SR Latch

 

- $S$  is “set” and  $R$  is “reset.”
- We will examine how the SR latch behaves for different values of  $S$  and  $R$ .

# SR Latches

$R(t)$	$S(t)$	$Q(t - \epsilon)$	$P(t - \epsilon)$	$Q(t + \epsilon)$	$P(t + \epsilon)$
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		

Analyze the circuit when the inputs are different.

# SR Latches

$R(t)$	$S(t)$	$Q(t - \varepsilon)$	$P(t - \varepsilon)$	$Q(t + \varepsilon)$	$P(t + \varepsilon)$
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	0	1

Analyze the circuit when the inputs are different.



# SR Latches

$R(t)$	$S(t)$	$Q(t - \epsilon)$	$P(t - \epsilon)$	$Q(t + \epsilon)$	$P(t + \epsilon)$
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		

Analyze the circuit when the inputs are both 0.

# SR Latches

$R(t)$	$S(t)$	$Q(t - \epsilon)$	$P(t - \epsilon)$	$Q(t + \epsilon)$	$P(t + \epsilon)$
0	0	0	0	1	1
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0

Analyze the circuit when the inputs are both 0.

# Stability of the SR Latch

- Notice that when  $R = S = 0$ , the values of  $P$  and  $Q$  are unstable when both are 0 or both are 1.

# Stability of the SR Latch

- Notice that when  $R = S = 0$ , the values of  $P$  and  $Q$  are unstable when both are 0 or both are 1.
- In reality, one of them receives the new value slightly ahead of the other, which then leads to stability.

# Stability of the SR Latch

- Notice that when  $R = S = 0$ , the values of  $P$  and  $Q$  are unstable when both are 0 or both are 1.
- In reality, one of them receives the new value slightly ahead of the other, which then leads to stability.
- But it may take a few moments to stabilize.

# SR Latches

$R(t)$	$S(t)$	$Q(t - \epsilon)$	$P(t - \epsilon)$	$Q(t + \epsilon)$	$P(t + \epsilon)$
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

Analyze the circuit when the inputs are both 1.

# SR Latches

$R(t)$	$S(t)$	$Q(t - \epsilon)$	$P(t - \epsilon)$	$Q(t + \epsilon)$	$P(t + \epsilon)$
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

Analyze the circuit when the inputs are both 1.

# SR Latches

## SR Latch

$R$	$S$	$Q$	$P$
0	0	0	1
0	0	1	0
0	1	1	0
1	0	0	1
1	1	0	0



# SR Latches

- If  $S$  is asserted (1) and  $R$  is deasserted (0), then  $Q$  is asserted (1), i.e.,  $Q$  is **set**.

# SR Latches

- If  $S$  is asserted (1) and  $R$  is deasserted (0), then  $Q$  is asserted (1), i.e.,  $Q$  is **set**.
- If  $R$  is asserted (1) and  $S$  is deasserted (0), then  $Q$  is deasserted (0), i.e.,  $Q$  is **reset**.

# SR Latches

- If  $S$  is asserted (1) and  $R$  is deasserted (0), then  $Q$  is asserted (1), i.e.,  $Q$  is **set**.
- If  $R$  is asserted (1) and  $S$  is deasserted (0), then  $Q$  is deasserted (0), i.e.,  $Q$  is **reset**.
- Thus, the name, set-reset latch.

# SR Latches

- If  $S$  is asserted (1) and  $R$  is deasserted (0), then  $Q$  is asserted (1), i.e.,  $Q$  is **set**.
- If  $R$  is asserted (1) and  $S$  is deasserted (0), then  $Q$  is deasserted (0), i.e.,  $Q$  is **reset**.
- Thus, the name, set-reset latch.
- If  $R$  and  $S$  are both 1, then the values of  $Q$  and  $P$  are 0. As we will see, this case will not arise.

# SR Latches

- In all but the last case (which will not arise),  $P = \overline{Q}$ . Therefore, we will rename it  $\overline{Q}$ .

# SR Latches

- In all but the last case (which will not arise),  $P = \overline{Q}$ . Therefore, we will rename it  $\overline{Q}$ .
- Note that when  $R$  and  $S$  are both deasserted (0),  $Q$  maintains its value (either 0 or 1) and  $\overline{Q}$  maintains the complementary value.

# SR Latches

- In all but the last case (which will not arise),  $P = \overline{Q}$ . Therefore, we will rename it  $\overline{Q}$ .
- Note that when  $R$  and  $S$  are both deasserted (0),  $Q$  maintains its value (either 0 or 1) and  $\overline{Q}$  maintains the complementary value.
- Thus, the SR Latch is able to *store* the values of  $Q$  and  $\overline{Q}$ .

# SR Latches

- In all but the last case (which will not arise),  $P = \overline{Q}$ . Therefore, we will rename it  $\overline{Q}$ .
- Note that when  $R$  and  $S$  are both deasserted (0),  $Q$  maintains its value (either 0 or 1) and  $\overline{Q}$  maintains the complementary value.
- Thus, the SR Latch is able to *store* the values of  $Q$  and  $\overline{Q}$ .
- The  $S$  input (set) will set  $Q$  and the  $R$  input (reset) will reset  $Q$ .



- How would the SR latch behave if we replaced the NOR gates with NAND gates?

# Outline

1 Sequential Circuits

2 SR Latches

**3 The Clock**

4 D Latches


5 D Flip Flops

6 Assignment

# The Clock


- The **clock** is a component of the processor whose value continuously oscillates between 0 and 1.
- As we will soon see, the clock is used to control all other components of the processor.

# The Clock

 


The behavior of the clock over time

# The Clock

 

On the rising edge, the clock changes from 0 to 1

# The Clock

 

On the falling edge, the clock changes from 1 to 0

# Outline

- 1 Sequential Circuits
- 2 SR Latches
- 3 The Clock
- 4 D Latches**
- 5 D Flip Flops
- 6 Assignment


# D Latches

- A **D** Latch is able to store a bit on the rising edge of the Clock.
- It uses an SR Latch to store the value and it uses a pair of AND-gates to initiate the storing when the clock switches from 0 to 1.
- It is a **clocked** circuit; one of its inputs is the clock.




# D Latches

## D Latch

 

# D Latches

## D Latch

 

# D Latches

- The input  $R/S$  is the data  $D$  to be stored.
- When  $\text{Clock} = 0$ , both AND gates will output 0.
- In this case, the latch is **closed**; the state of  $Q$  is unaffected.
- When  $\text{Clock} = 1$ , one of the AND gates will output 1, depending on the value of  $R/S$  (or  $D$ ).
- In this case, the latch is **open**; the value of  $D$  is stored as  $Q$ .
- Note that the two AND gates cannot both output 1 simultaneously.

# D Latches

- Suppose that initially  $\text{Clock} = 0$  and  $S/R = 1$ .
- Consider a sequence of events where  $\text{Clock}$  switches to 1, then 0, then 1 again.
- Suppose that after  $\text{Clock}$  changes back to 0,  $S/R$  changes to 0, and then  $\text{Clock}$  changes back to 1.
- What happen to  $Q$ ?


# D Latches

## D Latch


Clock = 0 and  $D = ?$  (*whatever*)

# D Latches

## D Latch

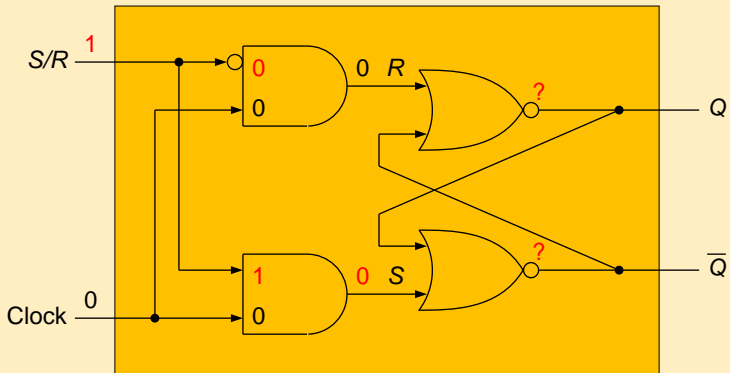


Change Clock to 1; Set  $Q$

 

# D Latches


## D Latch

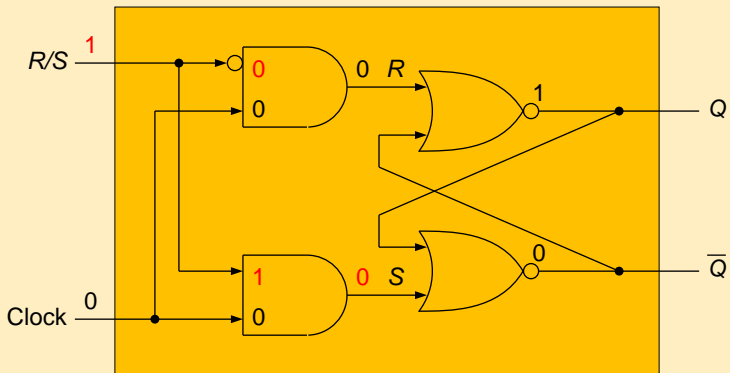

Change Clock to 0; no change to  $Q$

# D Latches

## D Latch

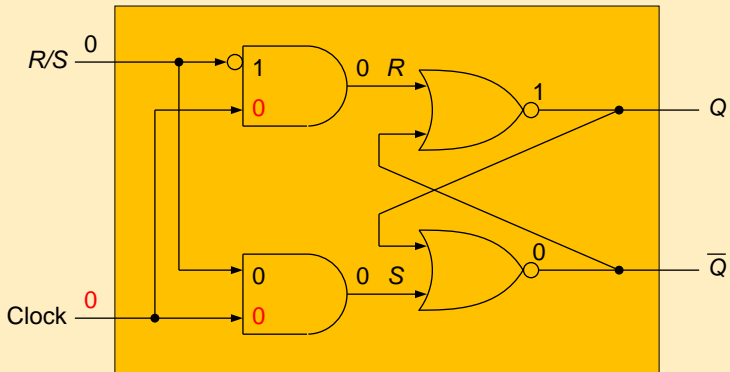


Change  $S/R$  to 0; no change to  $Q$



# D Latches


## D Latch

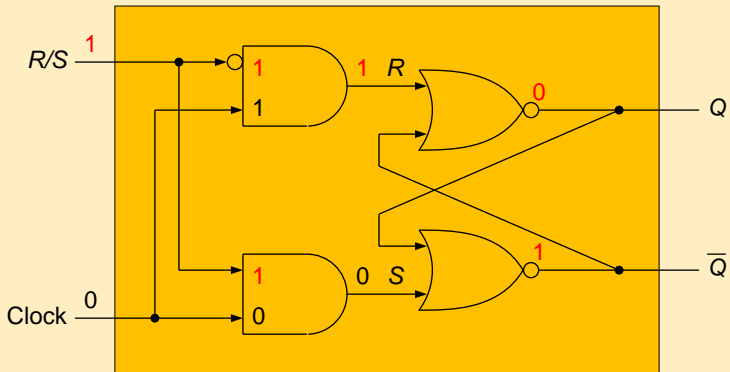

Change Clock to 1; Reset Q

# D Latches

## D Latch

 

The clock and the input and output of the D latch over time.

# D Latches

- The D Latch is **transparent** because when  $\text{Clock} = 1$ , the input  $D$  appears immediately as the output  $Q$ .

# D Latches


- How would we design a latch that *closes* on the rising edge and *opens* on the falling edge?

# Outline

- 1 Sequential Circuits
- 2 SR Latches
- 3 The Clock
- 4 D Latches
- 5 D Flip Flops**
- 6 Assignment

# D Flip Flops

## D Flip Flop

 

- The Clock will alternately set the value of the first latch or the second latch.

# D Flip Flops

## D Flip Flop



- Track the values of  $Q$  and  $\bar{Q}$  over time as the clock  $C$  and the input  $D$  changes.

# D Flip Flops

- **Set-up time** is the time it takes for data to stabilize before the rising clock edge.
- **Hold time** is the time the data must be stable after the rising clock edge.
- The value  $Q$  of the D Flip Flop is changed on the falling edge of the clock.



# D Flip Flops

- The D Flip Flop is not transparent.
- The input is stored when  $\text{Clock} = 1$ , but it appears as output only when  $\text{Clock} = 0$ .

# Outline

- 1 Sequential Circuits
- 2 SR Latches
- 3 The Clock
- 4 D Latches
- 5 D Flip Flops
- 6 Assignment**

# Assignment

## Assignment

- Read Section C.8.