

Digital Logic Circuits

Lecture 5 Section 2.4

Robb T. Koether

Hampden-Sydney College

Wed, Jan 22, 2014

1 Lewis Carroll's Logic Puzzles

2 Logic Gates

3 Normal Forms

4 Designing Circuits

5 Assignment

Outline

1 Lewis Carroll's Logic Puzzles

2 Logic Gates

3 Normal Forms

4 Designing Circuits

5 Assignment

Babies and Alligators

Babies and Alligators

- (a) All babies are illogical.
 - (b) Nobody is despised who can manage a crocodile.
 - (c) Illogical persons are despised.
-
- What conclusion can we draw from these premises?

Mermaids and Voyages

Mermaids and Voyages

- (a) None of the unnoticed things, met with at sea, are mermaids.
- (b) Things entered in the log, as met with at sea, are sure to be worth remembering.
- (c) I have never met with anything worth remembering, when on a voyage.
- (d) Things met with at sea, that are noticed, are sure to be recorded in the log.

- What conclusion can we draw from these premises?

Mermaids and Voyages

Mermaids and Voyages

- (a) No interesting poems are unpopular among people of real taste.
- (b) No modern poetry is free from affectation.
- (c) All your poems are on the subject of soap-bubbles.
- (d) No affected poetry is popular among people of real taste.
- (e) No ancient poem is on the subject of soap-bubbles.

- What conclusion can we draw from these premises?

Outline

- 1 Lewis Carroll's Logic Puzzles
- 2 Logic Gates**
- 3 Normal Forms
- 4 Designing Circuits
- 5 Assignment

Logic Gates

- There are three basic gates.
 - AND-gate
 - OR-gate
 - NOT-gate
- Two other gates.
 - NAND-gate
 - NOR-gate

AND-Gate

p	q	Output
1	1	1
1	0	0
0	1	0
0	0	0

- An AND-gate.
 - The output is 1 if both inputs are 1.
 - The output is 0 if either input is 0.

p	q	Output
1	1	1
1	0	1
0	1	1
0	0	0

- An OR-gate.
 - The output is 1 if either input is 1.
 - The output is 0 if both inputs are 0.

NOT-Gate

p	Output
1	0
0	1

- A NOT-gate.
 - The output is 1 if the input is 0.
 - The output is 0 if the input is 1.

NAND-Gate

p	q	Output
1	1	0
1	0	1
0	1	1
0	0	1

- An NAND-gate.
 - The output is 0 if both inputs are 1.
 - The output is 1 if either input is 0.

NOR-Gate

p	q	Output
1	1	0
1	0	0
0	1	0
0	0	1

- An NOR-gate.
 - The output is 0 if either input is 1.
 - The output is 1 if both inputs are 0.

Outline

1 Lewis Carroll's Logic Puzzles

2 Logic Gates

3 Normal Forms

4 Designing Circuits

5 Assignment

Disjunctive Normal Form

- A logical expression is in **disjunctive normal form** (DNF) if
 - It is a *disjunction* of clauses,
 - Each clause is a *conjunction* of variables and negations of variables.
 - Each variable or its negation appears in each clause exactly once.

Example

$$p \rightarrow q \equiv (p \wedge q) \vee (\sim p \wedge q) \vee (\sim p \wedge \sim q).$$

$$p \leftrightarrow q \equiv (p \wedge q) \vee (\sim p \wedge \sim q).$$

$$p \mid q \equiv (p \wedge \sim q) \vee (\sim p \wedge q) \vee (\sim p \wedge \sim q).$$

$$p \downarrow q \equiv \sim p \wedge \sim q.$$

- What are disjunctive normal forms for T and F?

Conjunctive Normal Form

- A logical expression is in **conjunctive normal form (CNF)** if
 - It is a *conjunction* of clauses,
 - Each clause is a *disjunction* of variables and negations of variables.
 - Each variable or its negation appears in each clause exactly once.

Example

$$p \rightarrow q \equiv \sim p \vee q.$$

$$p \leftrightarrow q \equiv (p \vee \sim q) \wedge (\sim p \vee q).$$

$$p \mid q \equiv \sim p \vee \sim q.$$

$$p \downarrow q \equiv (p \vee \sim q) \vee (\sim p \vee q) \vee (\sim p \vee \sim q).$$

- What are conjunctive normal forms for T and F?

Outline

- 1 Lewis Carroll's Logic Puzzles
- 2 Logic Gates
- 3 Normal Forms
- 4 Designing Circuits**
- 5 Assignment

Output Tables

Input		Output
1	1	0
1	0	1
0	1	0
0	0	0

- An **output table** shows the output of a logical function for every possible combination of inputs.

Designing Circuits

- To design a circuit that represents a logical function,
 - Write an output table for the circuit. The table reveals the DNF form of the function.
 - Write the logical expression and simplify it, if possible.
 - Draw the circuit using AND-gates, OR-gates, and NOT-gates (and NAND-gates and NOR-gates).

Example

Input		Output
1	1	0
1	0	1
0	1	0
0	0	0

- Design a circuit for the above function (which is $\sim (p \rightarrow q)$).

Example

- Design a circuit for $(p \rightarrow q) \wedge (q \leftrightarrow \sim r)$.

Example

Input			Output
p	q	r	
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	0
0	1	0	1
0	0	1	1
0	0	0	0

- Produce the output table for $(p \rightarrow q) \wedge (q \leftrightarrow \sim r)$.

Example

- Based on the output table, the DNF of

$$(p \rightarrow q) \wedge (q \leftrightarrow \sim r)$$

is

$$(p \wedge q \wedge \sim r) \vee (\sim p \wedge q \wedge \sim r) \vee (\sim p \wedge \sim q \wedge r).$$

- I do not see any way to simplify this.
- Draw the circuit.

Example

- Design a logic circuit for

$$(p \wedge q) \vee (\sim q \wedge \sim r) \vee r.$$

- Use the *conjunctive* normal form of

$$(p \wedge q) \vee (\sim q \wedge \sim r) \vee r$$

to design a circuit.

Outline

- 1 Lewis Carroll's Logic Puzzles
- 2 Logic Gates
- 3 Normal Forms
- 4 Designing Circuits
- 5 Assignment**

Assignment

Assignment

- Read Section 2.4, pages 64 - 75.
- Exercises 1, 2, 5, 6, 9, 10, 15, 17, 18, 19, 24, 25, 32, page 76.